
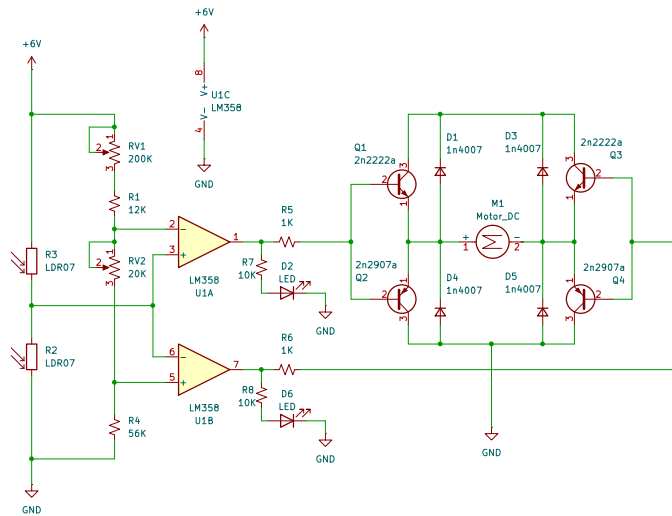


Motor Control Circuit

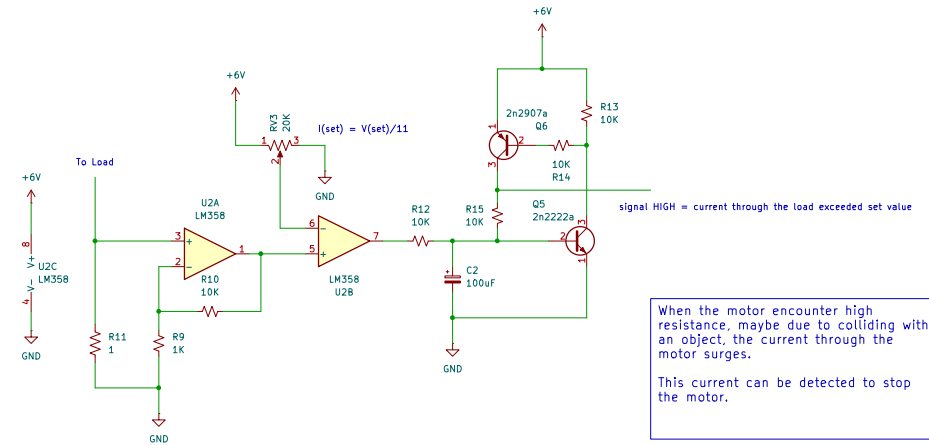

(Need one circuit for each motor)

Current Level Detector (Used as replacement to mechanical limit switches)



Work in progress :)